

Two Hardware Description Languages

■ Verilog

- developed in 1984 by Gateway Design Automation
- became an IEEE standard (1364) in 1995
- More popular in US

■ VHDL (VHSIC Hardware Description Language)

- Developed in 1981 by the Department of Defense
- Became an IEEE standard (1076) in 1987
- More popular in Europe

■ In this course we will use Verilog

Defining a module

- A module is the main building block in Verilog
- We first need to declare:
 - Name of the module
 - Types of its connections (input, output)
 - Names of its connections



Defining a module

```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
  
endmodule
```



A question of style

The following two codes are identical

```
module test ( a, b, y );  
    input a;  
    input b;  
    output y;  
  
endmodule
```

```
module test ( input a,  
              input b,  
              output y );  
  
endmodule
```

What if we have busses?

- You can also define multi-bit busses.

- [range_start : range_end]

- Example:

```
input  [31:0] a;    // a[31], a[30] .. a[0]
output [15:8] b1;   // b1[15], b1[14] .. b1[8]
output [7:0]  b2;   // b2[7], b2[6] .. b1[0]
input                clk; // single signal
```

Basic Syntax

- **Verilog is case sensitive:**
 - `SomeName` and `somename` are not the same!
- **Names cannot start with numbers:**
 - `2good` is not a valid name
- **Whitespace is ignored**

```
// Single line comments start with a //  
  
/* Multiline comments  
   are defined like this */
```

Good Practices

- **Develop/use a consistent naming style**
- **Use MSB to LSB ordering for busses (little-endian)**
 - Try using “**a[31:0]**” and not “**a[0:31]**”
- **Define one module per file**
 - Makes managing your design hierarchy easier
- **Use a file name that equals module name**
 - i.e. module **TryThis** is defined in a file called **TryThis.v**

There are Two Main Styles of HDL

■ Structural


- Describe how modules are interconnected
- Each module contains other modules (instances)
- ... and interconnections between these modules
- Describes a hierarchy

■ Behavioral

- The module body contains functional description of the circuit
- Contains logical and mathematical operators

■ Practical circuits would use a combination of both

Structural HDL: Instantiating a Module

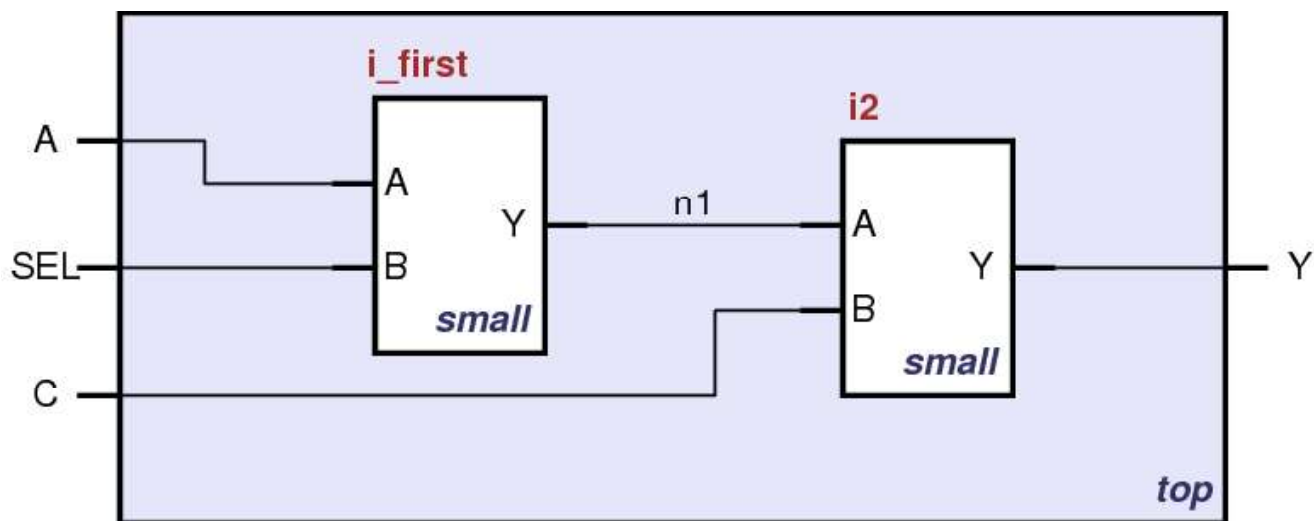


Structural HDL Example

Module Definitions

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```


```
endmodule
```

Structural HDL Example

Module Definitions

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```


```
endmodule
```

Structural HDL Example

Wire definitions

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```


Structural HDL Example

Instantiate first module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
  // instantiate small once  
  small i_first ( .A(A),  
                  .B(SEL),  
                  .Y(n1) );
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
  // description of small
```

```
endmodule
```

Structural HDL Example


Instantiate second module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
  // instantiate small once  
  small i_first ( .A(A),  
                  .B(SEL),  
                  .Y(n1) );
```

```
  // instantiate small second time  
  small i2 ( .A(n1),  
             .B(C),  
             .Y(Y) );
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```


```
  // description of small
```

```
endmodule
```

Structural HDL Example

Short Instantiation
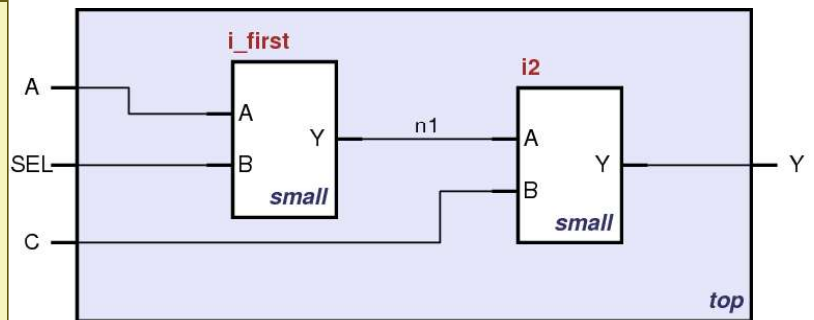
```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // alternative  
  small i_first ( A, SEL, n1 );  
  
  /* Shorter instantiation,  
   pin order very important */  
  
  // any pin order, safer choice  
  small i2 ( .B(C),  
            .Y(Y),  
            .A(n1) );  
  
endmodule
```



```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

What Happens with HDL code?

■ Automatic Synthesis

- Modern tools are able to map a behavioral HDL code into gate-level schematics
- They can perform many optimizations
- ... however they can not guarantee that a solution is optimal
- Most common way of Digital Design these days


■ Simulation

- Allows the behavior of the circuit to be verified without actually manufacturing the circuit
- Simulators can work on behavioral or gate-level schematics


Behavioral HDL: Defining Functionality

```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
    assign y = ~a & ~b & ~c |  
               a & ~b & ~c |  
               a & ~b & c;  
  
endmodule
```

Behavioral HDL: Synthesis Results

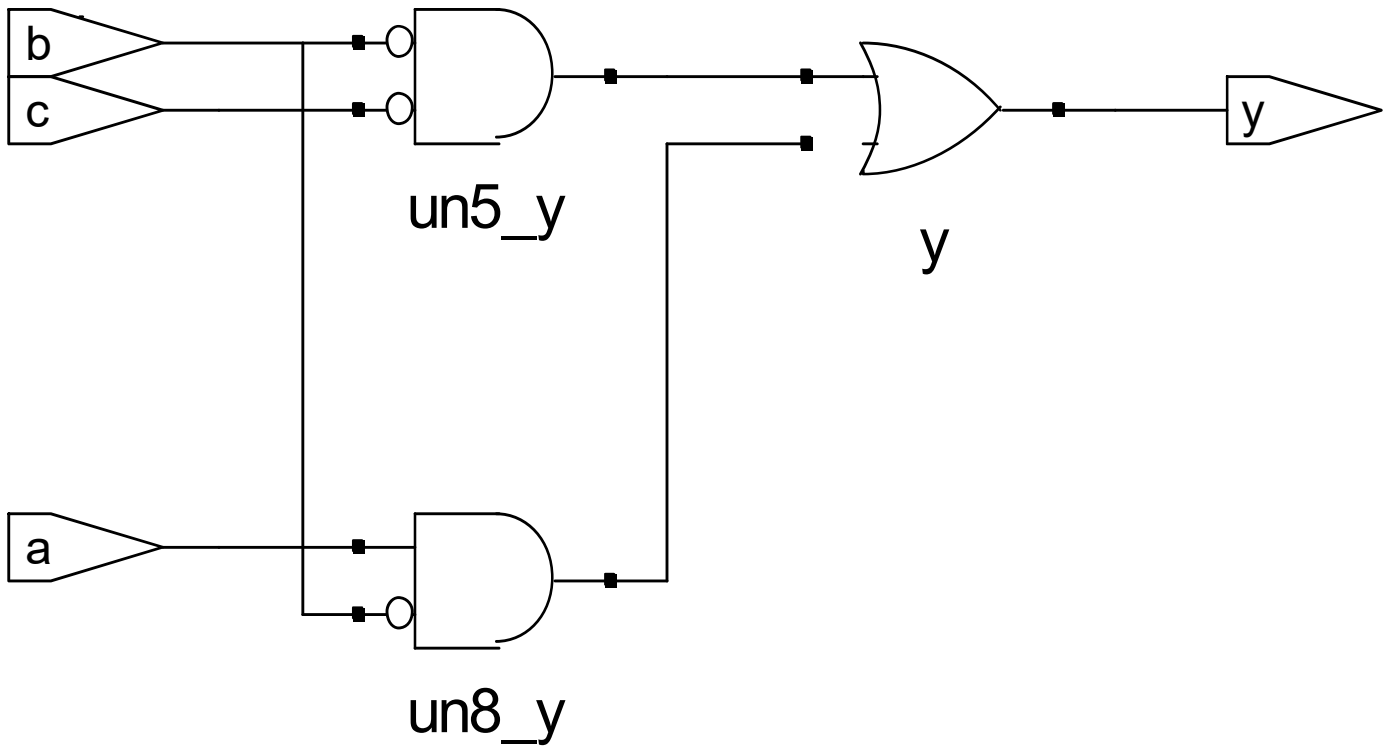

Behavioral HDL: Simulating the Circuit

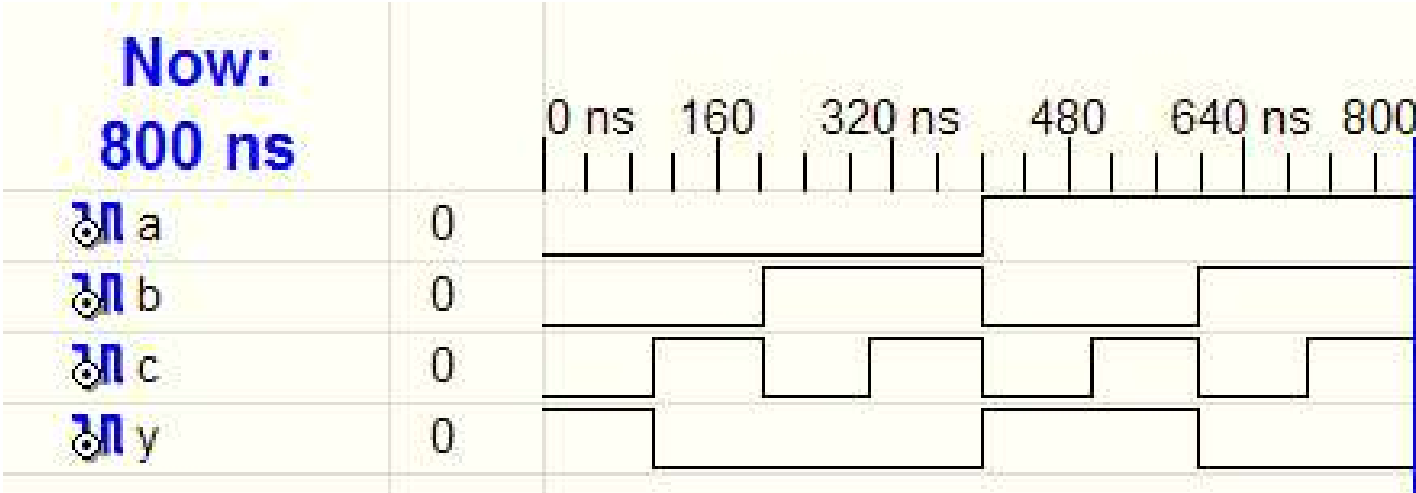

Bitwise Operators


```
module gates(input  [3:0]  a, b,
              output [3:0] y1, y2, y3, y4, y5);

    /* Five different two-input logic
       gates acting on 4 bit busses */

    assign y1 = a & b;      // AND
    assign y2 = a | b;      // OR
    assign y3 = a ^ b;      // XOR
    assign y4 = ~(a & b);   // NAND
    assign y5 = ~(a | b);   // NOR

endmodule
```


Bitwise Operators: Synthesis Results

 

Reduction Operators

```
module and8(input  [7:0] a,  
            output  y);  
  
    assign y = &a;  
  
    // &a is much easier to write than  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    //             a[3] & a[2] & a[1] & a[0];  
  
endmodule
```

Reduction Operators: assign y = &a;

 


Conditional Assignment

```
module mux2(input [3:0] d0, d1,  
            input    s,  
            output [3:0] y);  
  
    assign y = s ? d1 : d0;  
    // if (s) then y=d1 else y=d0;  
  
endmodule
```

- **? :** is also called a **ternary operator** as it operates on three inputs:
 - s
 - d1
 - d0.

 Conditional Assignment: $y = s ? d1 : d0;$



More Conditional Assignments

```
module mux4(input  [3:0] d0, d1, d2, d3
            input  [1:0] s,
            output [3:0] y);

    assign y = s[1] ? ( s[0] ? d3 : d2)
               : ( s[0] ? d1 : d0);

    // if (s1) then
    //     if (s0) then y=d3 else y=d2
    // else
    //     if (s0) then y=d1 else y=d0

endmodule
```

Even More Conditional Assignments

```
module mux4(input  [3:0] d0, d1, d2, d3
            input  [1:0] s,
            output [3:0] y);

    assign y = (s == 2'b11) ? d3 :
               (s == 2'b10) ? d2 :
               (s == 2'b01) ? d1 :
               d0;

    // if      (s = "11" ) then y= d3
    // else if (s = "10" ) then y= d2
    // else if (s = "01" ) then y= d1
    // else                                y= d0

endmodule
```

How to Express numbers ?

N' Bxx

8' b0000_0001

- **(N) Number of bits**

- Expresses how many bits will be used to store the value

- **(B) Base**

- Can be b (binary), h (hexadecimal), d (decimal), o (octal)

- **(xx) Number**

- The value expressed in base, apart from numbers it can also have X and Z as values.
- Underscore _ can be used to improve readability

Number Representation in Verilog

Verilog	Stored Number	Verilog	Stored Number
4' b1001	1001	4' d5	0101
8' b1001	0000 1001	12' hFA3	1111 1010 0011
8' b0000_1001	0000 1001	8' o12	00 001 010
8' bxX0X1zZ1	XX0X 1ZZ1	4' h7	0111
'b01	0000 .. 0001	12' h0	0000 0000 0000

What have seen so far:

- **Describing structural hierarchy with Verilog**
 - Instantiate modules in an other module
- **Writing simple logic equations**
 - We can write AND, OR, XOR etc
- **Multiplexer functionality**
 - If ... then ... else
- **We can describe constants**
- **But there is more:**

Precedence of operations in Verilog

Highest

~	NOT
*, /, %	mult, div, mod
+, -	add,sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
?:	ternary operator

Lowest

Example: Comparing two numbers

An XNOR gate

```
module MyXnor (input a, b,  
               output z);  
  
    assign z = ~(a ^ b); //not XOR  
  
endmodule
```

An AND gate

```
module MyAnd (input a, b,  
              output z);  
  
    assign z = a & b;    // AND  
  
endmodule
```


Example: Comparing Two Numbers

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                 output eq);
    wire c0, c1, c2, c3, c01, c23;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    MyAnd haha (.A(c0), .B(c1), .Z(c01) ); // AND
    MyAnd hoho (.A(c2), .B(c3), .Z(c23) ); // AND
    MyAnd bubu (.A(c01), .B(c23), .Z(eq) ); // AND

endmodule
```

Example: Comparing Two Numbers

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                 output eq);
    wire c0, c1, c2, c3, c01, c23;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    assign c01 = c0 & c1;
    assign c23 = c2 & c3;
    assign eq  = c01 & c23;

endmodule
```

Example: Comparing Two Numbers

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                 output eq);
    wire c0, c1, c2, c3;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR

    assign eq  = c0 & c1 & c2 & c3;

endmodule
```

Example: Comparing Two Numbers

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                 output eq);
    wire [3:0] c; // bus definition

    MyXnor i0 (.A(a0), .B(b0), .Z(c[0])) ; // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c[1])) ; // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c[2])) ; // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c[3])) ; // XNOR

    assign eq  = &c; // short format

endmodule
```

Example: Comparing Two Numbers

```
module compare (input [3:0] a, input [3:0] b,  
                output eq);  
    wire [3:0] c; // bus definition  
  
    MyXnor i0 (.A(a[0]), .B(b[0]), .Z(c[0])) ; // XNOR  
    MyXnor i1 (.A(a[1]), .B(b[1]), .Z(c[1])) ; // XNOR  
    MyXnor i2 (.A(a[2]), .B(b[2]), .Z(c[2])) ; // XNOR  
    MyXnor i3 (.A(a[3]), .B(b[3]), .Z(c[3])) ; // XNOR  
  
    assign eq  = &c; // short format  
  
endmodule
```

Example: Comparing Two Numbers

```
module compare (input [3:0] a, input [3:0] b,  
                output eq);  
    wire [3:0] c; // bus definition  
  
    assign c = ~(a ^ b); // XNOR  
  
    assign eq = &c; // short format  
  
endmodule
```

Example: Comparing Two Numbers

```
module compare (input [3:0] a, input [3:0] b,  
                output eq);  
  
    assign eq = (a == b) ? 1 : 0; // really short  
  
endmodule
```

What is the BEST way of writing Verilog

- Quite simply **IT DOES NOT EXIST!**
- **Code should be easy to understand**
 - Sometimes longer code is easier to comprehend
- **Hierarchy is very useful**
 - In the previous example it did not look like that, but for larger designs it is indispensable
- **Try to stay closer to hardware**
 - After all the goal is to design hardware